




Digital Logic
Design with FPGA

Digital Design with VHDL

Introduction




VHDL description

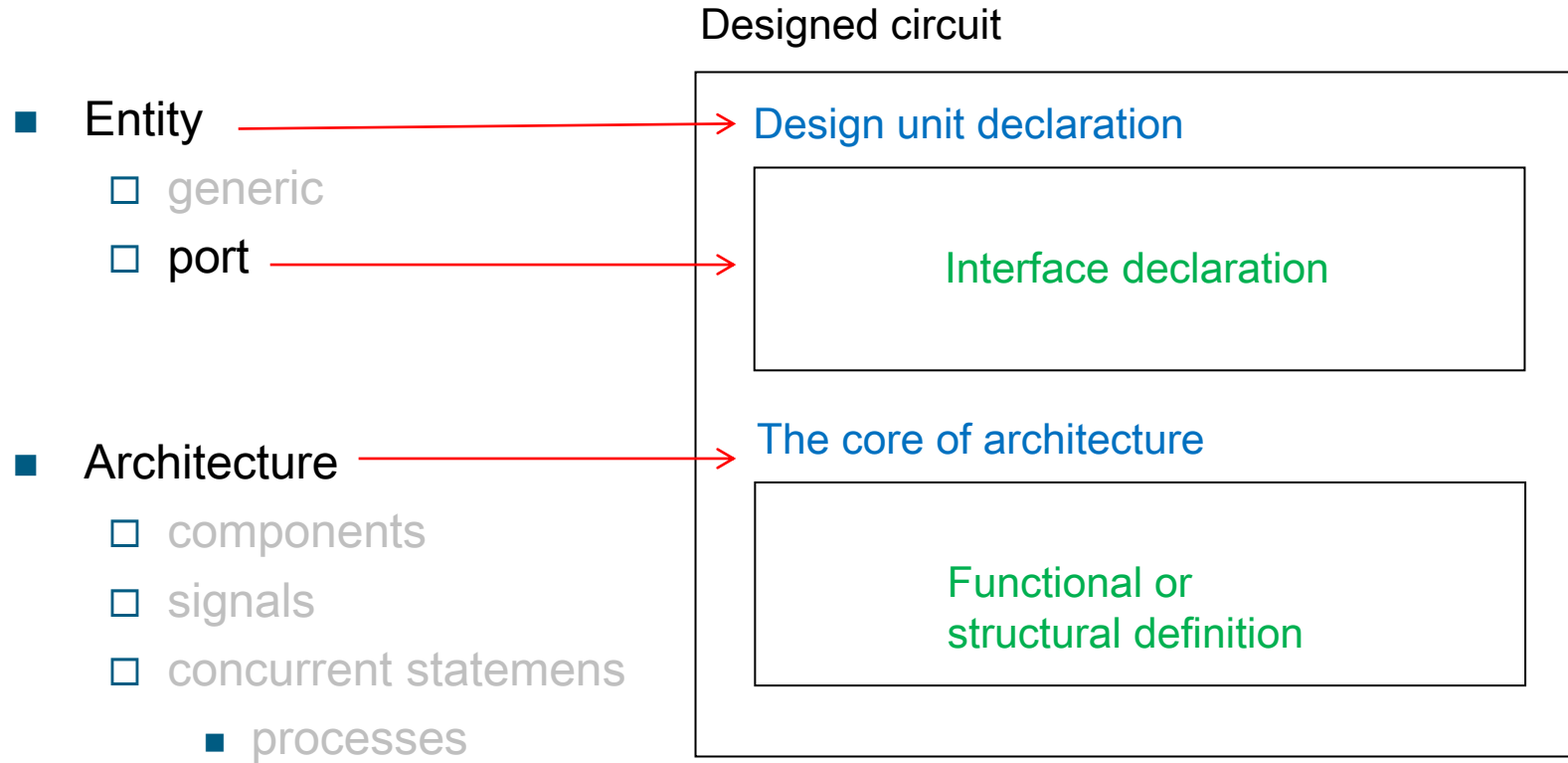





VHDL descriptions of basic logic

 

 
```
entity Inverter is
  port ( A: in bit;
         X: out bit );
end entity Inverter;
architecture NOTfunction of Inverter is
begin
  X <= not A;
end architecture NOTfunction;
```


 
```
entity ANDgate is
  port ( A, B: in bit;
         X: out bit );
end entity ANDgate;
architecture ANDfunction of ANDgate is
begin
  X <= A and B;
end architecture ANDfunction;
```



 
```
entity NANDgate is
  port ( A, B, C: in bit;
         X: out bit );
end entity NANDgate;
architecture NANDfunction of NANDgate is
begin
  X <= A nand B nand C;
end architecture NANDfunction;
```



```
entity XNORgate is
  port ( A, B: in bit;
         X: out bit );
end entity XNORgate;
architecture XNORfunction of XNORgate is
begin
  X <= A xnor B;
end architecture XNORfunction;
```



VHDL descriptions of basic logic

 

```
12 entity ANDgate is
13     port ( A, B: in bit;
14           X: out bit );
15 end entity ANDgate;
16 architecture ANDfunction of ANDgate is
17 begin
18     X <= A and B;
19 end architecture ANDfunction;
```

```
2  entity ANDgateN is
3     port ( A, B: in bit_vector(7 downto 0);
4           X: out bit_vector(7 downto 0) );
5 end entity ANDgateN;
6
7  architecture ANDfunction of ANDgateN is
8  begin
9     X <= A and B;
10 end architecture ANDfunction;
```

```
13 entity ANDgateG is
14     generic(N: natural := 8);
15     port ( A, B: in bit_vector(N-1 downto 0);
16           X: out bit_vector(N-1 downto 0) );
17 end entity ANDgateG;
18
19 architecture ANDfunction of ANDgateG is
20 begin
21     X <= A and B;
22 end architecture ANDfunction;
```




Basic parameters of digital logic

- Propagation delay time (t_p)

the time interval between the transition of an input pulse and the occurrence of the resulting transition of the output pulse

- t_{PHL} : the time between a specified reference point on the input pulse and a corresponding reference point on the resulting output pulse, with the output changing from the HIGH level to the LOW level (HL)
- t_{PLH} : The time between a specified reference point on the input pulse and a corresponding reference point on the resulting output pulse, with the output changing from the LOW level to the HIGH level (LH)

 



Basic parameters of digital logic

- **DC supply voltage** (V_{CC})
 - the typical dc supply voltage for CMOS logic is either 5V, 3.3V, 2.5V, or 1.8V, depending on the category
 - 5V CMOS fixed-logic can tolerate supply from 2V to 6V and still operate properly
 - 3.3V CMOS can operate with supply voltages from 2V to 3.6V
- **Power dissipation** (P_D) - product of the dc supply voltage and the average supply current; supply current when the gate output is LOW is greater than when the gate output is HIGH

$$P_D = V_{CC} \left(\frac{I_{CCH} + I_{CCL}}{2} \right)$$

- power dissipation of CMOS is dependent on the frequency of operation
- at zero frequency the **quiescent power** is typically in the microwatt/gate range (fixed-logic HC: 2.75 uW/gate at 0 Hz (quiescent) and 600 uW/gate at 1 MHz)
- power dissipation for bipolar gates is independent of frequency (fixed-logic ALS: 1.4 mW/gate regardless of the frequency; F: 6 mW/gate)



Basic parameters of digital logic

- **Speed-Power Product (SPP)**

can be used as a measure of the performance of a logic circuit taking into account the propagation delay time and the power dissipation

$$SPP = t_p P_D$$

- **Fan-Out**


the maximum number of inputs of the next stage that can be connected to one output of a gate made in the same technology (gate still maintain the output voltage levels within specified limits)

- Fan-out is specified in terms of **unit loads**

 - Example:

fixed-logic 74LS00 NAND,
current from a LOW input (I_{IL}) of a gate is 0,4mA
and the current that a LOW output (I_{OL})
can accept is 8,0mA

$$\text{unit loads} = \frac{I_{OL}}{I_{IL}} = \frac{8,0 \text{ mA}}{0,4 \text{ mA}} = 20$$





Digital Logic
Design with FPGA

Digital Design with VHDL

Combinational Logic





Outline

- Half and Full Adders
- Comparators
- Decoders
- Encoders
- Code Converters
- Multiplexers (Data Selectors)
- Demultiplexers
- Parity Generators/Checkers



Half-Adder

  - The half-adder accepts **two binary digits** on its inputs and produces two binary digits on its outputs - a **sum** bit and a **carry** bit.



Half-adder truth table.

A	B	C _{out}	Σ
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0



Σ = sum
C_{out} = output carry
A and B = input variables (operands)

```
10 entity halfA is port(  
11     a,b:    in std_logic;  
12     s,c:    out std_logic);  
13 end halfA;  
14 -----  
15 architecture df of halfA is  
16 begin  
17     s <= a xor b after 2 ns;  
18     c <= a and b after 1 ns;  
19 end df;
```



Full-Adder

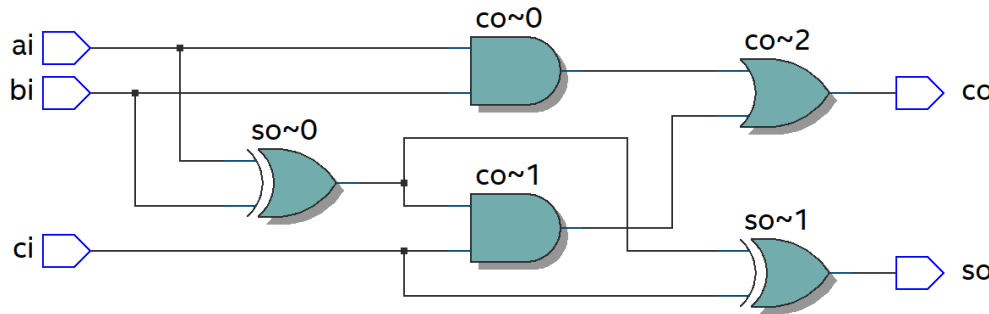 - The full-adder accepts two input bits and an input carry and generates a sum output and an output carry.



Full-adder truth table.

A	B	C _{in}	C _{out}	Σ
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

C_{in} = input carry, sometimes designated as CI
C_{out} = output carry, sometimes designated as CO
Σ = sum
A and B = input variables (operands)


```
5 entity fullA is port(  
6     ai,bi,ci:  in std_logic;  
7     so,co:    out std_logic);  
8 end fullA;  
9  
10 architecture gates of fullA is  
11  
12 begin  
13     so <= (ai xor bi) xor ci;  
14     co <= (ai and bi) or ((ai xor bi) and ci);  
15 end gates;
```



Full-Adder

- Arrangement of two half-adders to form a full-adder
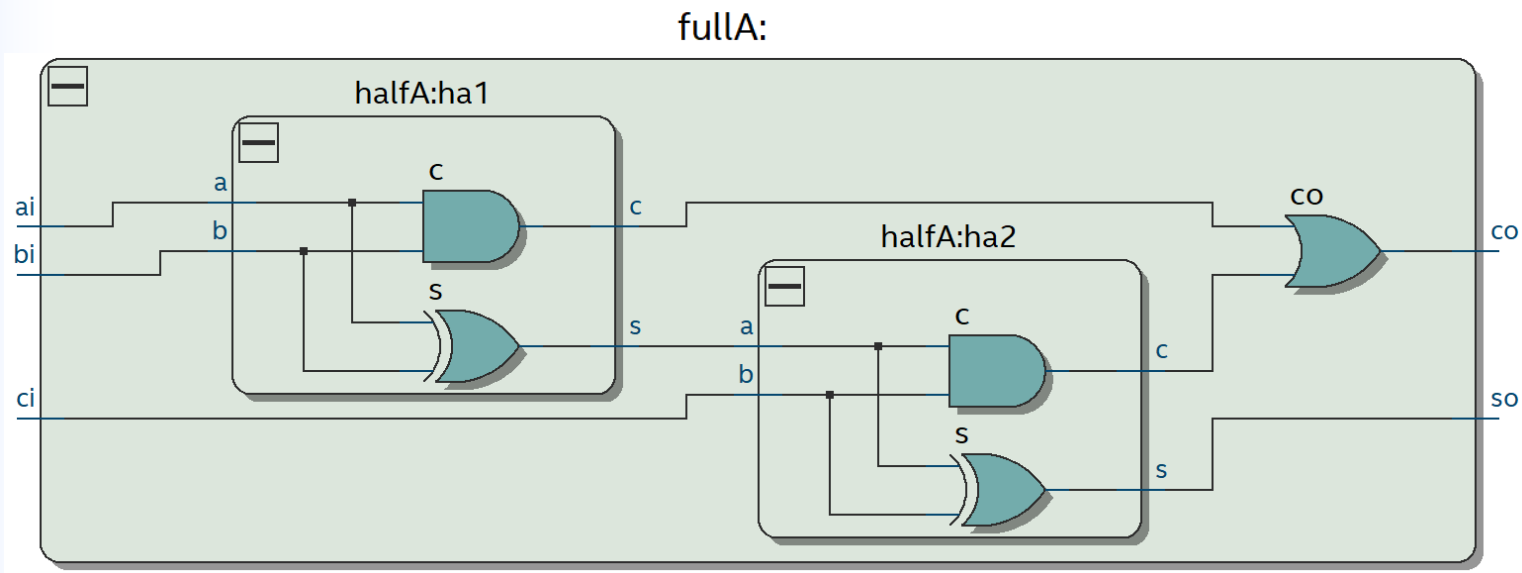
```
10 entity halfA is port(  
11     a,b:    in std_logic;  
12     s,c:    out std_logic);  
13 end halfA;
```



```
26 entity fullA is port(  
27     ai,bi,ci:  in std_logic;  
28     so,co:    out std_logic);  
29 end fullA;  
30 -----  
31 architecture mix of fullA is  
32     signal ha1s,ha1c,ha2c: std_logic;  
33 begin  
34     ha1: entity work.halfA(df)  
35         port map(ai,bi,ha1s,ha1c);  
36     ha2: entity work.halfA(df)  
37         port map(ha1s,ci,so,ha2c);  
38     co <= ha1c or ha2c after 1 ns;  
39 end mix;
```




Parallel Binary Adder

```
26 entity fullA is port(  
27     ai,bi,ci:  in std_logic;  
28     so,co:  out std_logic);  
29 end fullA;
```

```
46 entity adderN is  
47     generic (N: integer:=4);  
48     port(  
49         ai,bi:  in std_logic_vector(N-1 downto 0):=(others=>'0');  
50         ci:  in std_logic;  
51         so:  out std_logic_vector(N-1 downto 0);  
52         co:  out std_logic);  
53 end adderN;
```
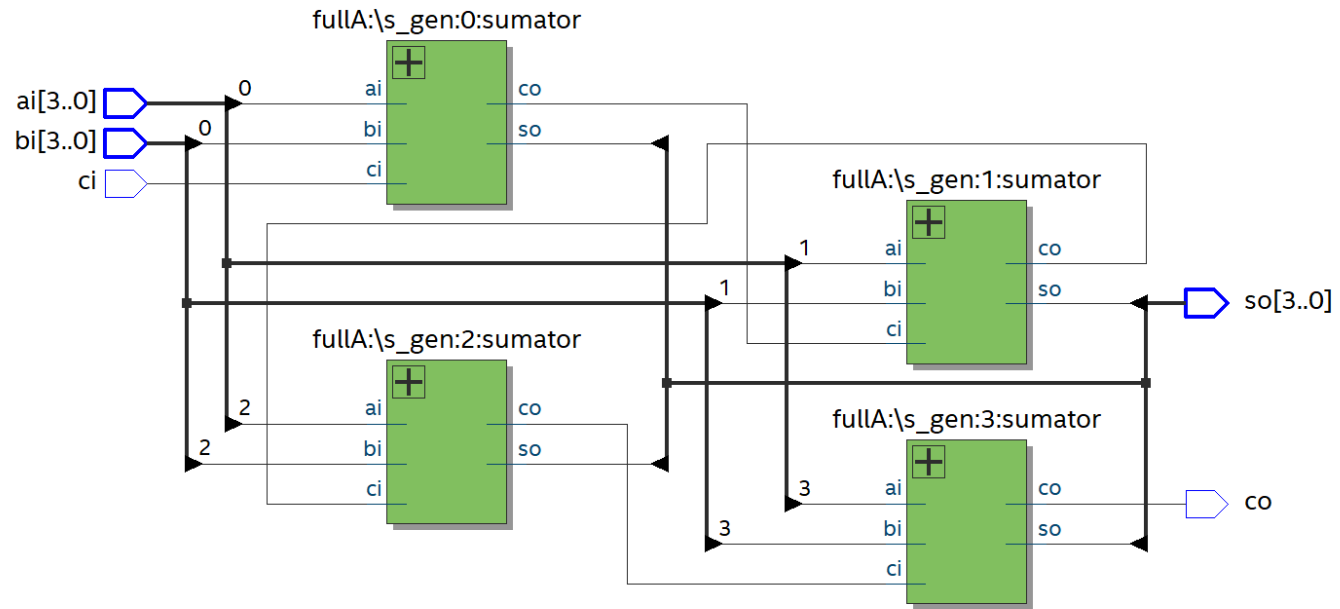
```
55 architecture generacja of adderN is  
56     signal carry: std_logic_vector(N downto 0):=(others=>'0');  
57     begin  
58         carry(0) <= ci;  
59         co <= carry(N);  
60     s_gen: for i in (N-1) downto 0 generate  
61         sumator:entity work.fullA(mix)  
62             port map(ai(i),bi(i),carry(i),so(i),carry(i+1));  
63     end generate;  
64     end generacja;
```





Parallel Binary Adder – FPGA implementation

```
46 entity adderN is
47     generic (N: integer:=64);
48     port(
49         ai,bi: in std_logic_vector(N-1 downto 0):=(others=>'0');
50         ci: in std_logic;
51         so: out std_logic_vector(N-1 downto 0);
52         co: out std_logic);
53 end adderN;
54
55 architecture structural of adderN is
56     signal carry: std_logic_vector(N downto 0):=(others=>'0');
57 begin
58     carry(0) <= ci;
59     co <= carry(N);
60     s_gen: for i in (N-1) downto 0 generate
61         sumator:entity work.fullA(mix)
62             port map(ai(i),bi(i),carry(i),so(i),carry(i+1));
63         end generate;
64 end structural;
```

```
17 entity adder64 is
18     Port ( a : in  STD_LOGIC_VECTOR (63 downto 0);
19           b : in  STD_LOGIC_VECTOR (63 downto 0);
20           s : out STD_LOGIC_VECTOR (63 downto 0);
21           ci: in std_logic;
22           co : out std_logic);
23 end adder64;
24
25 architecture Behavioral of adder64 is
26     signal s_i : std_logic_vector (64 downto 0);
27     signal a_i, b_i : std_logic_vector (64 downto 0);
28
29 begin
30     -- ins
31     a_i <= ('0' & a);
32     b_i <= ('0' & b);
33     -- func
34     s_i <= a_i + b_i + ci;
35     -- outs
36     s <= s_i(63 downto 0);
37     co <= s_i(64);
38 end Behavioral;
```

FPGA Device Utilization:

- 4-input LUTs: **320**
- Maximum path delay: **160ns**


64
11ns




Comparator

- Basic function of a comparator is to compare the magnitudes of two binary quantities to determine the relationship of those quantities
- In simplest form, a comparator circuit determines whether two numbers are equal

- Equality

 

- Inequality

 


To determine an inequality of binary numbers A and B:

- If A3 = 1 and B3 = 0, number A is greater than number B.
- If A3 = 0 and B3 = 1, number A is less than number B.
- If A3 = B3, then you must examine the next lower bit position for an inequality.



Comparator - VHDL

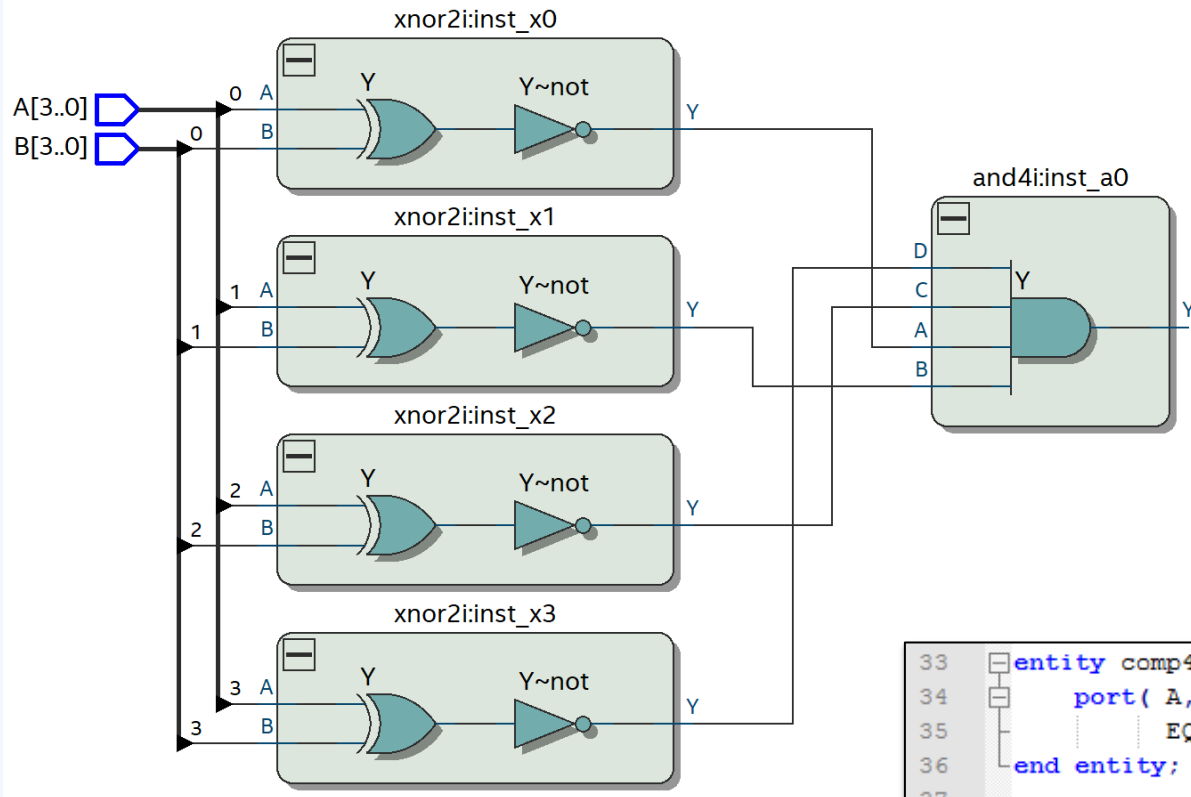


```
19 entity xnor2 is
20     port ( A, B: in std_logic;
21           Y: out std_logic );
22 end entity xnor2;
23
24 architecture behavior of xnor2 is
25 begin
26     Y <= not (A xor B);
27 end architecture behavior;
```

```
5 entity and4 is
6     port ( A, B, C, D: in std_logic;
7           Y: out std_logic );
8 end entity and4;
9
10 architecture behavior of and4 is
11 begin
12     Y <= A and B and C and D;
13 end architecture behavior;
```

```
33 entity comp4eq is
34     port( A, B: in std_logic_vector(3 downto 0);
35           EQ: out std_logic );
36 end entity;
37
38 architecture struct of comp4eq is
39     signal xout: std_logic_vector(A'range);
40
41 begin
42     inst_x0: entity work.xnor2 port map(A=>A(0), B=>B(0), Y=>xout(0) );
43     inst_x1: entity work.xnor2 port map(A=>A(1), B=>B(1), Y=>xout(1) );
44     inst_x2: entity work.xnor2 port map(A=>A(2), B=>B(2), Y=>xout(2) );
45     inst_x3: entity work.xnor2 port map(A=>A(3), B=>B(3), Y=>xout(3) );
46     inst_a0: entity work.and4
47         port map(A=>xout(0), B=>xout(1), C=>xout(2), D=>xout(3), Y=>EQ);
48 end architecture;
```




Comparator - VHDL

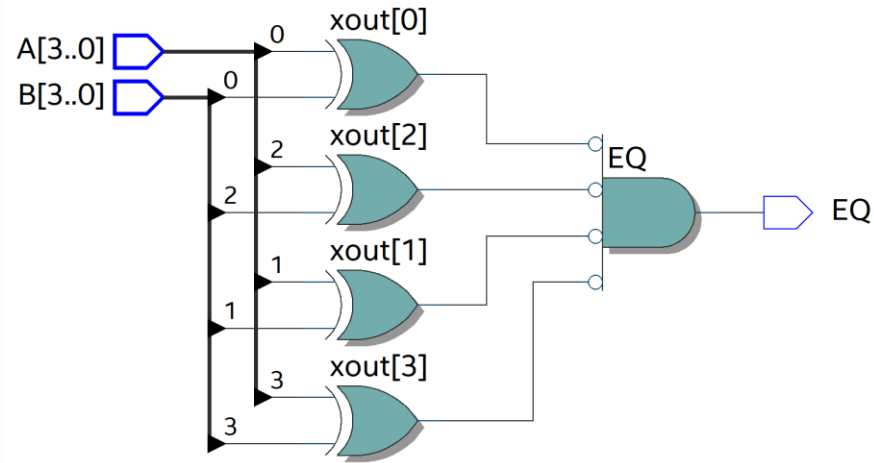

```
6  entity comp4eq is
7      port( A, B: in std_logic_vector(3 downto 0);
8            EQ: out std_logic );
9  end entity;
10
11 architecture behav of comp4eq is
12     signal xout: std_logic_vector(A'range);
13 begin
14     EQ <= xout(3) and xout(1) and xout(2) and xout(0);
15     xout <= A xnor B;
16 end architecture;
```

```
23 entity compNeq is
24     generic(N: positive := 32);
25     port( A, B: in std_logic_vector(N-1 downto 0);
26           EQ: out std_logic );
27 end entity;
28
29 architecture behav of compNeq is
30
31 begin
32     EQ <= '1' when (A=B) else '0';
33 end architecture;
```



Comparator – FPGA implementation

4-input LUTs

```
39  entity compN is
40      generic(N: positive := 32);
41      port( A, B: in std_logic_vector(N-1 downto 0);
42           EQ, AthenB, BthenA: out std_logic );
43  end entity;
44
45  architecture behav1 of compN is
46      signal xout: std_logic_vector(2 downto 0);
47  begin
48      EQ<=xout(2); AthenB<=xout(1); BthenA<=xout(0);
49      xout <= "100" when (A=B) else
50           "010" when (A>B) else
51           "001" when (A<B) else
52           "000";
53  end architecture;
```

■ 82


```
55  architecture behav2 of compN is
56      signal eqi: std_logic:='0';
57  begin
58      eqi <= '1' when (A=B) else '0';
59      AthenB <= '1' when (A>B) else '0';
60      BthenA <= '0' when (A>B) else (not eqi);
61      EQ <= eqi;
62  end architecture;
```

■ 50



Decoder

 - A **decoder** is a digital circuit that detects the presence of a specified combination of bits (code) on its inputs
- In general form, a decoder has **n input lines** to handle n bits and from **one to 2^n output lines** to indicate the presence of one or more n-bit combinations





```
1  library ieee;
2  use ieee.std_logic_1164.all;
3  use ieee.std_logic_unsigned.all;
4
5  entity simple_decoder is
6  port ( A: in std_logic_vector(3 downto 0);
7        Y: out std_logic );
8  end entity simple_decoder;
9
10 architecture nine of simple_decoder is
11 begin
12     Y <= A(3) and (not A(2)) and (not A(1)) and A(0);
13 end architecture nine;
```



BCD-2-Decimal

- converts each BCD code (8421 code) into one of ten possible decimal digit indications
- frequently referred as a *4-line-to-10-line decoder* or a *1-of-10 decoder*


```
15 library IEEE;
16 use IEEE.STD_LOGIC_1164.ALL;
17
18 entity bcd2dec is
19     Port ( bcd : in std_logic_vector(3 downto 0);
20           dec : out std_logic_vector(9 downto 0));
21 end entity bcd2dec;
22
23 architecture Behavioral of bcd2dec is
24 begin
25     with bcd select
26         dec <= "1111111110" when "0000",    --0
27                "1111111101" when "0001",    --1
28                "1111111011" when "0010",    --2
29                "1111110111" when "0011",    --3
30                "1111101111" when "0100",    --4
31                "1111011111" when "0101",    --5
32                "1110111111" when "0110",    --6
33                "1101111111" when "0111",    --7
34                "1011111111" when "1000",    --8
35                "0111111111" when "1001",    --9
36                "1111111111" when others;    --
37 end architecture Behavioral;
```

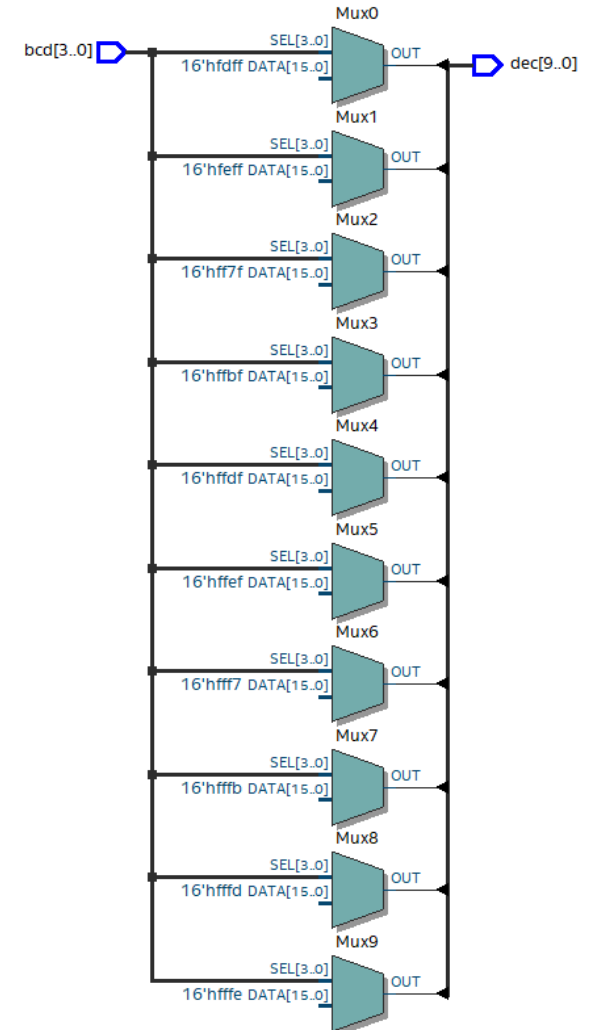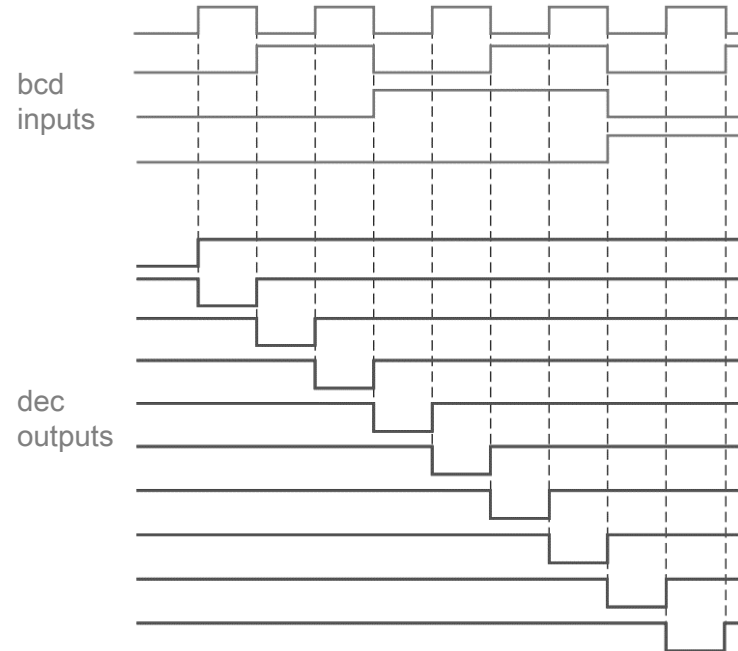



BCD-2-7Segment

 - The BCD-to-7-segment decoder accepts the BCD code on its inputs and provides outputs to drive 7-segment display devices to produce a decimal readout




	seg_out(6:0)						
	g	f	e	d	c	b	a
1	1	1	1	1	0	0	1
2	0	1	0	0	1	0	0
3	0	1	1	0	0	0	0
4	0	0	1	1	0	0	1
5	0	0	1	0	0	1	0
6	0	0	0	0	0	1	0
7	1	1	1	1	0	0	0
8	0	0	0	0	0	0	0
9	0	0	1	0	0	0	0
0	1	0	0	0	0	0	0

```

42 entity dec7seg is
43     Port ( bcd : in std_logic_vector(3 downto 0);
44           seg : out std_logic_vector(6 downto 0)); --low
45 end entity dec7seg;
46
47 architecture ttable of dec7seg is
48 begin
49     with bcd select
50         seg<= "1111001" when x"1",           --      0
51              "0100100" when x"2",           -- 5|      |1
52              "0110000" when x"3",           -- | 6 |
53              "0011001" when x"4",           --      7
54              "0010010" when x"5",           -- 4|      |2
55              "0000010" when x"6",           -- |      |
56              "1111000" when x"7",           --      8
57              "0000000" when x"8",           --      3
58              "0010000" when x"9",
59              "1000000" when x"0",
60              "0111111" when others;
61 end architecture ttable;

```

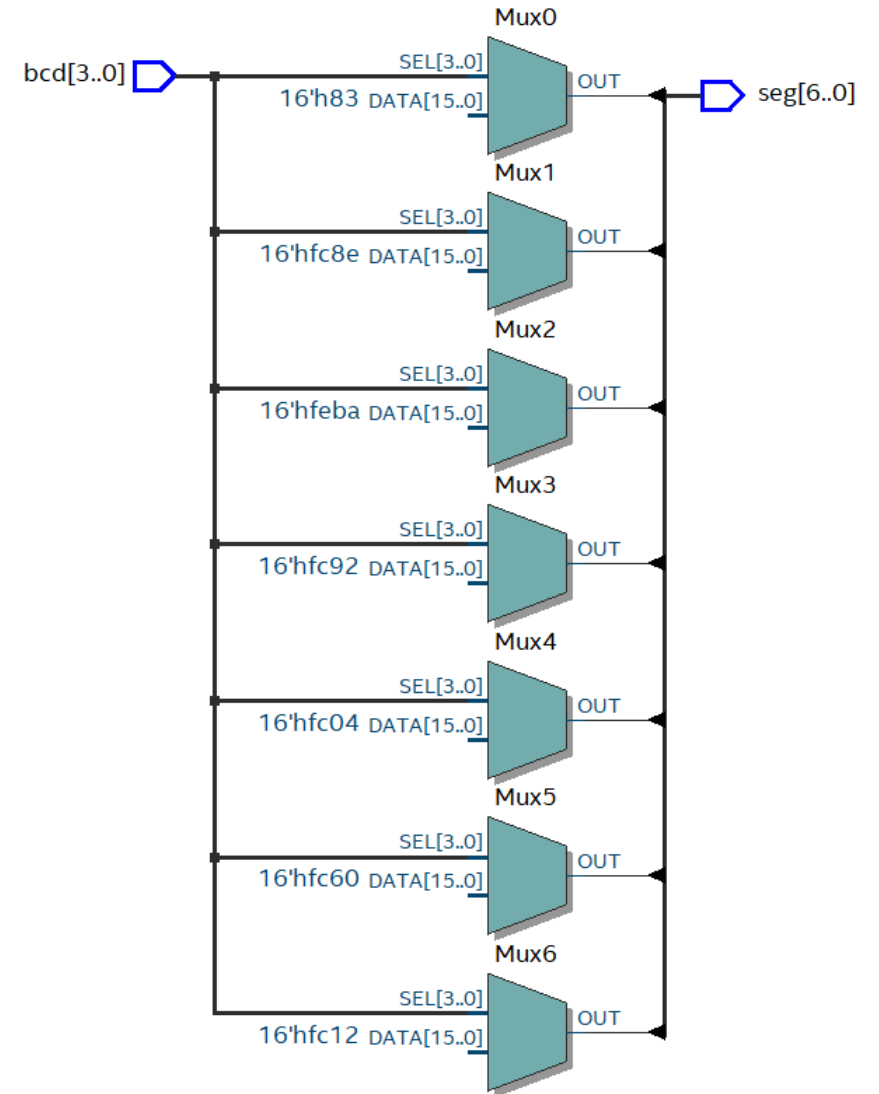




Encoders

- An **encoder** is a combinational logic circuit that performs a “reverse” decoder function
- Accepts an active level on one of its inputs representing a digit and converts it to a coded output, such as BCD or binary


Decimal Digit	BCD Code			
	A ₃	A ₂	A ₁	A ₀
0	0	0	0	0
1	0	0	0	1
2	0	0	1	0
3	0	0	1	1
4	0	1	0	0
5	0	1	0	1
6	0	1	1	0
7	0	1	1	1
8	1	0	0	0
9	1	0	0	1

 


```
5 entity encoder is
6   Port ( dec : in std_logic_vector(9 downto 0);
7         bcd : out std_logic_vector(3 downto 0));
8 end entity encoder;
9
10 architecture equation of encoder is
11 begin
12   bcd(0) <= dec(1) or dec(3) or dec(5) or dec(7) or dec(9);
13   bcd(1) <= dec(2) or dec(3) or dec(6) or dec(7);
14   bcd(2) <= dec(4) or dec(5) or dec(6) or dec(7);
15   bcd(3) <= dec(8) or dec(9);
16 end architecture;
```



Code Converters

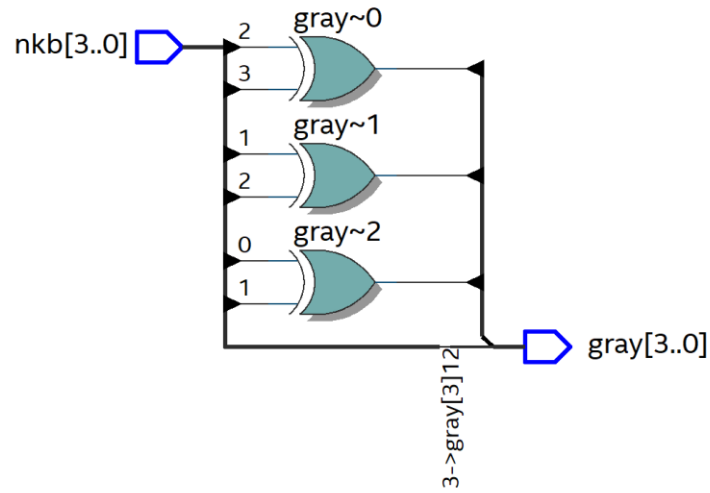
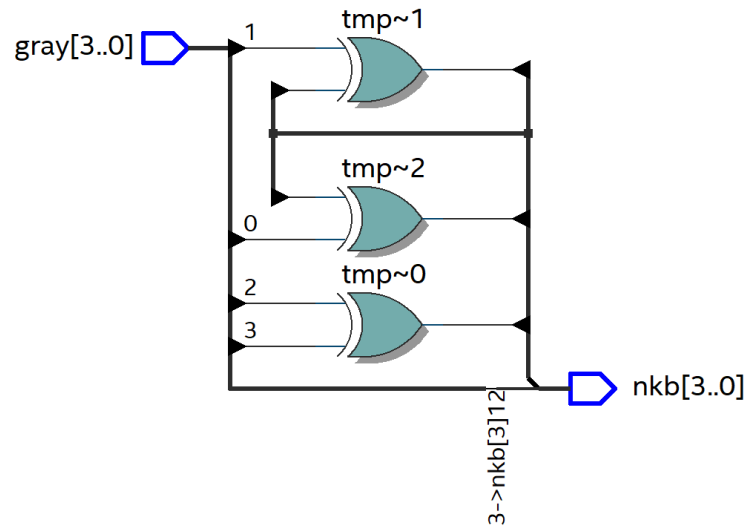
```
4 entity nkb2gray is
5   Port ( nkb : in  STD_LOGIC_VECTOR (3 downto 0); -- 0-1sb
6         gray : out STD_LOGIC_VECTOR (3 downto 0)
7         );
8 end nkb2gray;
9
10 architecture Behavioral of nkb2gray is
11
12 begin
13   gray(3) <= nkb(3);
14   gray(2) <= nkb(2) xor nkb(3);
15   gray(1) <= nkb(1) xor nkb(2);
16   gray(0) <= nkb(0) xor nkb(1);
17
18 end Behavioral;
```




```
4 entity gray2nkb is
5   Port ( gray : in  STD_LOGIC_VECTOR (3 downto 0); -- 0-1sb
6         nkb : out STD_LOGIC_VECTOR (3 downto 0)
7         );
8 end gray2nkb;
9
10 architecture Behavioral of gray2nkb is
11   signal tmp: std_logic_vector(3 downto 0);
12
13 begin
14   nkb <= tmp;
15   tmp(3) <= gray(3);
16   tmp(2) <= tmp(3) xor gray(2);
17   tmp(1) <= tmp(2) xor gray(1);
18   tmp(0) <= tmp(1) xor gray(0);
19
20 end Behavioral;
```



Multiplexer


 
- A multiplexer (MUX) is a device that allows digital information from several sources to be routed onto a single line
- Multiplexers are also known as data selectors



Data selection for a 1-of-4-multiplexer.

Data-Select Inputs		Input Selected
S_1	S_0	
0	0	D_0
0	1	D_1
1	0	D_2
1	1	D_3
  
$$Y = D_0\bar{S}_1\bar{S}_0 + D_1\bar{S}_1S_0 + D_2S_1\bar{S}_0 + D_3S_1S_0$$







Multiplexer

```
5 entity mux4x1 is
6   Port ( d0,d1,d2,d3 : in std_logic;
7         s0,s1 : std_logic;
8         y : out std_logic);
9 end entity mux4x1;
```

```
11 architecture equation of mux4x1 is
12 begin
13   y <= (d0 and (not s1 and not s0) ) or
14        (d1 and (not s1 and s0) ) or
15        (d2 and ( s1 and not s0) ) or
16        (d3 and ( s1 and s0) );
17 end architecture;
```

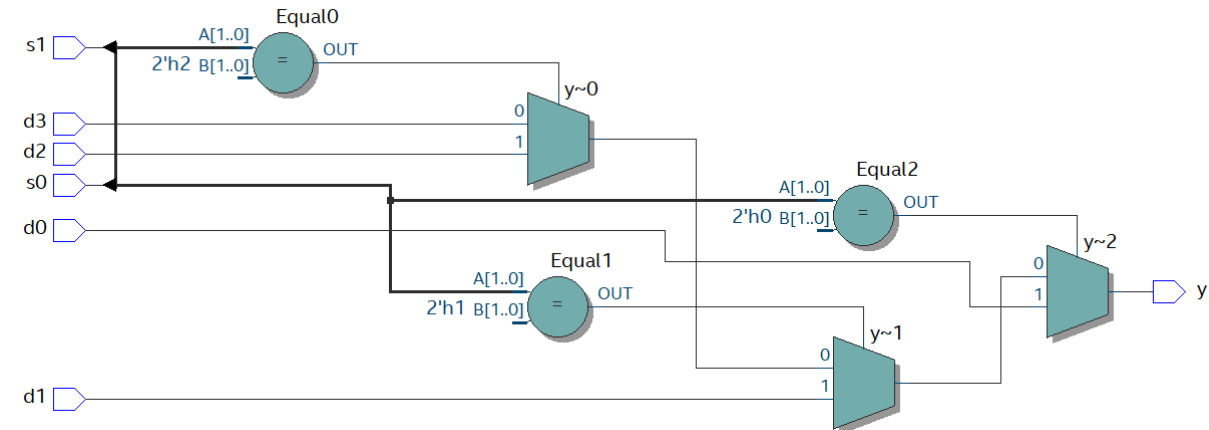
 
```
19 architecture behav of mux4x1 is
20   signal sel: std_logic_vector(1 downto 0);
21 begin
22   y <= d0 when (sel="00") else
23        d1 when (sel="01") else
24        d2 when (sel="10") else
25        d3 ;
26   sel <= s1 & s0;
27 end architecture;
```





Demultiplexer

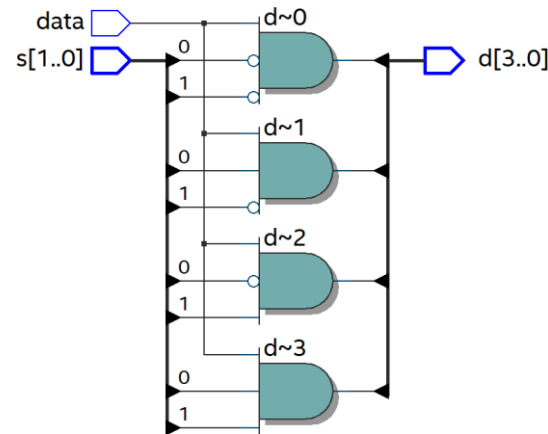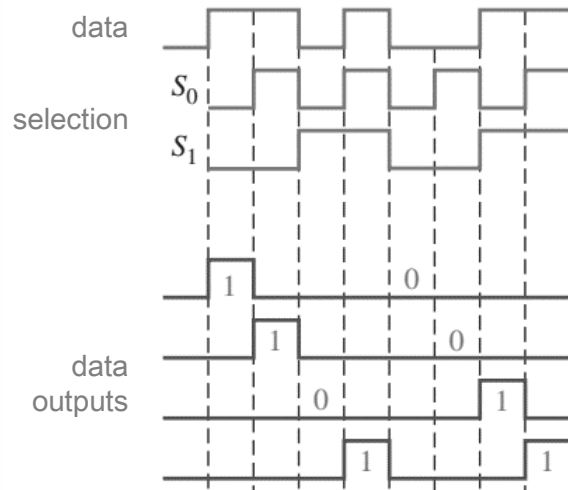- A demultiplexer (DEMUX) basically reverses the multiplexing function. It takes digital information from one line and distributes it to a given number of output lines
- The demultiplexer is also known as a data distributor
- Decoders can also be used as demultiplexers




```
5 entity demux is
6     Port ( data : in std_logic;
7           s : in std_logic_vector(1 downto 0);
8           d : out std_logic_vector(3 downto 0));
9 end entity demux;
10
11 architecture equation of demux is
12     signal invs : std_logic_vector(1 downto 0);
13 begin
14     d(0) <= data and ( invs(0) and invs(1) );
15     d(1) <= data and ( s(0) and invs(1) );
16     d(2) <= data and ( invs(0) and s(1) );
17     d(3) <= data and ( s(0) and s(1) );
18     invs <= not s;
19 end architecture;
```



Demultiplexer

- The demultiplexer is also known as a data distributor
- Decoders can also be used as demultiplexers

```
6 entity demux2 is
7   generic (delay: time := 3 ns);
8   port (s: in std_logic_vector(1 downto 0);
9         din: in std_logic_vector(3 downto 0);
10        y: out std_logic_vector(15 downto 0) );
11 end entity demux2;
12
13 architecture with_delay of demux2 is
14   signal y_tmp: std_logic_vector(y'range);
15 begin
16   y <= y_tmp after delay;
17   y_tmp(3 downto 0) <= din when (s=0) else x"0";
18   y_tmp(7 downto 4) <= din when (s=1) else x"0";
19   y_tmp(11 downto 8) <= din when (s=2) else x"0";
20   y_tmp(15 downto 12) <= din when (s=3) else x"0";
21
22 end architecture with_delay;
```

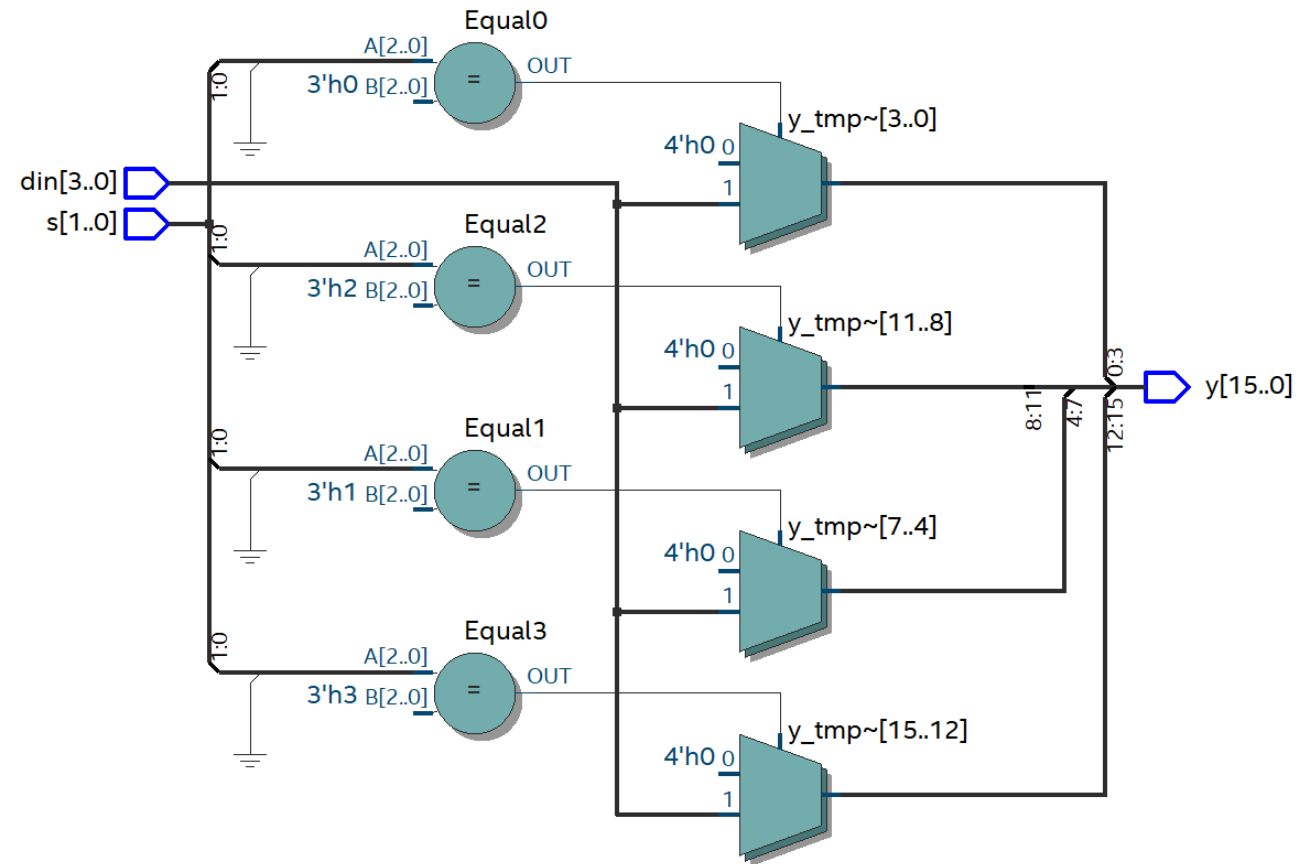



Logic Function Generator

A useful application of the data selector/multiplexer is in the generation of combinational logic functions in sum-of-products form

- Case 1: $F(A,B,C,D) = \Sigma\{0,1,3,4,5,7,9,10,13,14\}$


	A	B	C	D	F
0	0	0	0	0	1
1	0	0	0	1	1
2	0	0	1	0	
3	0	0	1	1	1
4	0	1	0	0	1
5	0	1	0	1	1
6	0	1	1	0	
7	0	1	1	1	1
8	1	0	0	0	
9	1	0	0	1	1
10	1	0	1	0	1
11	1	0	1	1	
12	1	1	0	0	
13	1	1	0	1	1
14	1	1	1	0	1
15	1	1	1	1	

$F_0(AB=00) = \neg C \text{ or } D$

$F_1(AB=01) = \neg C \text{ or } D$

$F_2(AB=10) = \neg CD \text{ and } C/D$

$F_3(AB=11) = \neg CD \text{ and } C/D$

 



Logic Function Generator

Case 2: $F(A,B,C,D) = \Sigma\{0,1,3,4,5,7,9,10,13,14\}$

- determining the form of the minimal function
- selection of address variables
- determining equations for data inputs

		CD			
		00	01	11	10
AB	00	1	1	1	0
	01	1	1	1	0
	11	0	1	0	1
	10	0	1	0	1



1.

$$F = \begin{aligned} &/A/C + \\ &/AD + \\ &/CD + \\ &AC/D \end{aligned}$$

A	B	C	D
0	X	0	X
0	X	X	1
X	X	0	1
1	X	1	0
1	4	1	1

sel={A,C}
data={B,D}


2.

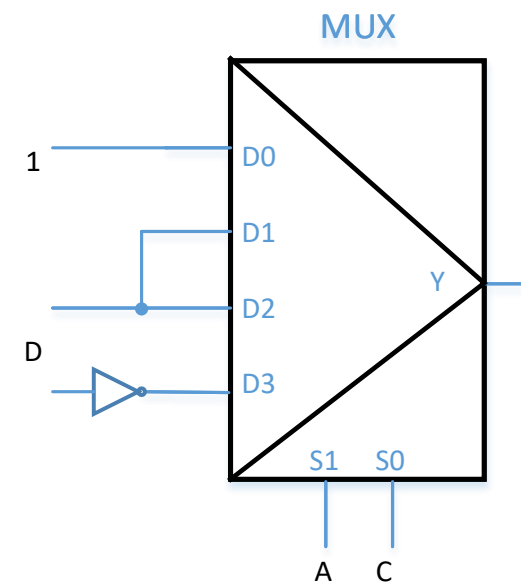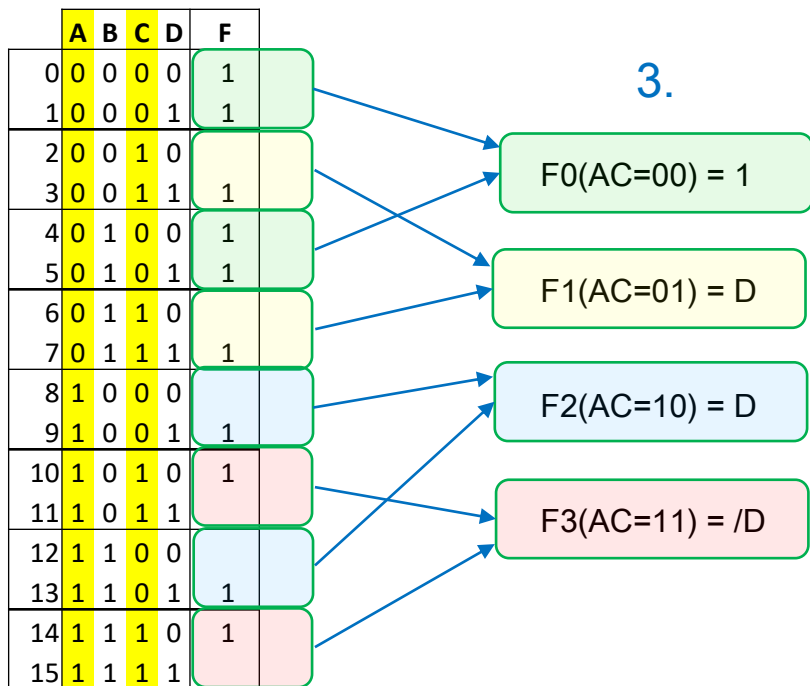



Basic Parity Logic

 
- A parity bit indicates if the number of 1s in a code is even or odd for the purpose of error detection.
- The sum (disregarding carries) of an even number of 1s is always 0, and the sum of an odd number of 1s is always 1.



Summing of four bits

- 10-bits parity checker
 
```
4 entity ParityCheck is
5     port(a0, a1, a2, a3, a4, a5, a6, a7, a8, a9: in std_logic;
6           x: out std_logic);
7 end ParityCheck;
8
9 architecture gates of ParityCheck is
10 begin
11     x <= ((a0 xor a1) xor (a2 xor a3)) xor
12          ((a4 xor a5) xor (a6 xor a7)) xor
13          (a8 xor a9);
14 end gates;
```





Basic Parity Logic

```
4 entity reduced_xor is
5     generic(WIDTH: natural:=8);
6     port(a: in std_logic_vector(WIDTH-1 downto 0);
7         y: out std_logic);
8 end reduced_xor;
9
10 architecture gen_if_arch of reduced_xor is
11     signal tmp: std_logic_vector(WIDTH-2 downto 1);
12 begin
13     xor_gen: for i in 1 to (WIDTH-1) generate
14         left_gen: if i=1 generate -- leftmost stage
15             tmp(i) <= a(i) xor a(0);
16         end generate;
17         middle_gen: if (1<i) and (i < (WIDTH-1)) generate -- middle stages
18             tmp(i) <= a(i) xor tmp(i-1);
19         end generate;
20         right_gen: if i=(WIDTH-1) generate -- rightmost stage
21             y <= a(i) xor tmp(i-1);
22         end generate;
23     end generate;
24 end gen_if_arch;
```

