



Embedded Systems
Hardware Design

RTL implementation




RTL architecture

Register Transfer Level (RTL) description is a lower level of abstraction than behavioral description but higher level abstraction than netlist description of a circuit design. As shown in last section, RTL description is written using either Verilog or VHDL (using any of their flavors). In RTL description, circuit is described in terms of registers (flip-flops or latches) and the data is transferred between them using logical operations (combinational logic, if needed) and that is why the nomenclature: Register Transfer Level (RTL).



4-bit counter with overflow

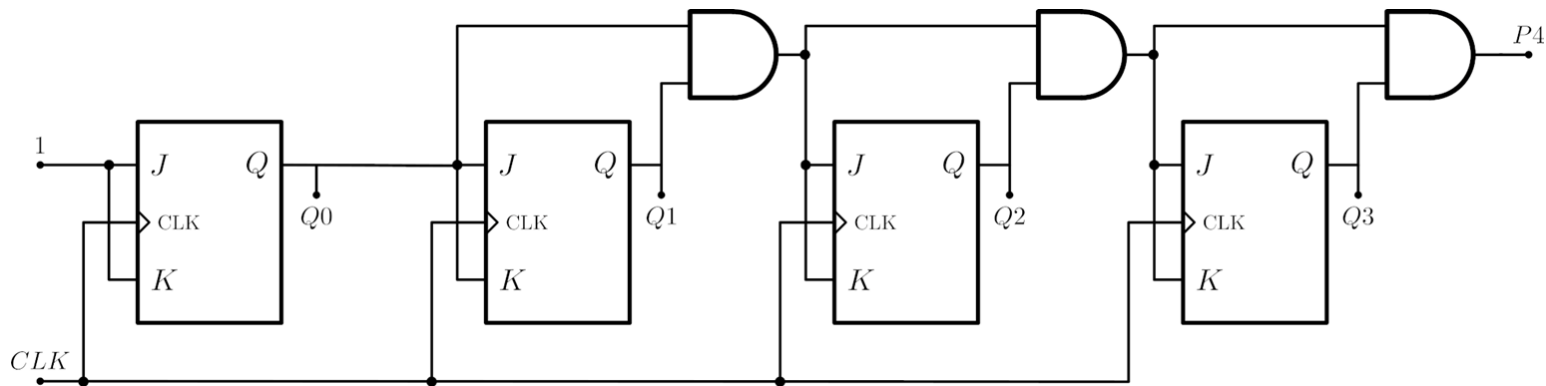Example of RTL architecture is 4-bit counter presented below. As you can see between each logic gate you can find JK Flip-Flop. The structure of this counter results from the principle of its operation. The next slide shows the code describing the operation of the counter in verilog using the RTL description.





Behavioral implementation

```
module counter( input clk,
                output [3:0] q,
                output p);
    reg [3:0] count;
    always@(posedge clk)
    begin
count <= count + 1;
    end
    assign q = count;
    assign p = (count==15) ? 1'b1 : 1'b0;
endmodule
```



Testbench

```
module tb_counter;

    reg clk;
    wire [3:0]q;
    wire p;

    counter u0 ( .clk(clk),
                .q(q),
                .p(p));

    initial begin
        $dumpfile("test.vcd");
        $dumpvars;
        clk = 1;
        #320 $finish;
    end

    always #10 clk=~clk;always #20 $display("%d %d",p,q);

endmodule
```



Simulation

Compiling tb.v file:

```
verilator --trace --binary -j 0 tb.v
```

Running the simulation:

```
./obj_dir/Vtb
```



Results of the counter simulation

0 0

0 1

0 2

0 3

0 4

0 5

0 6

0 7

0 8

0 9

0 10

0 11

0 12

0 13

0 14

1 15

- tb.v:16: Verilog \$finish

0 0

0 1

0 2

0 3

0 4

0 5

0 6

0 7

0 8

0 9

0 10

0 11

0 12

0 13

0 14


1 15

- tb.v:16: Verilog \$finish



Results of the counter simulation

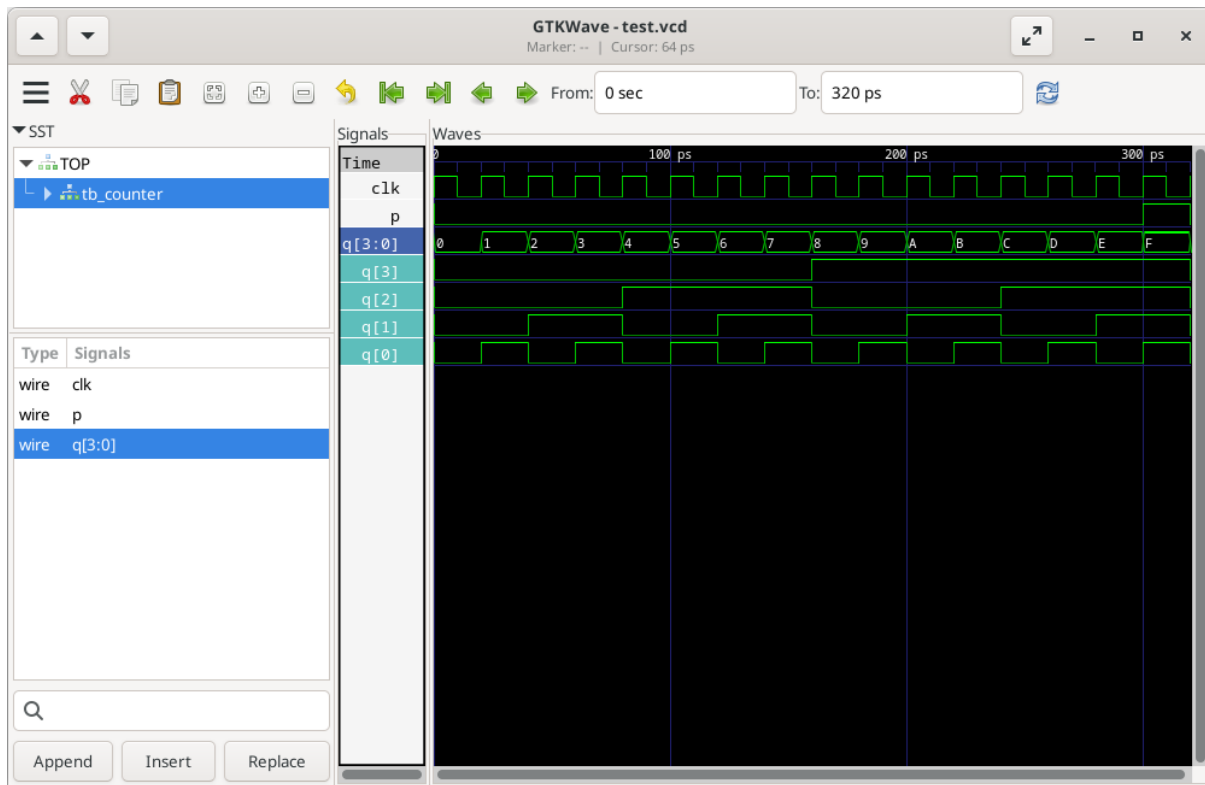
The image below presents results of simulation in the time domain.





Pipelining

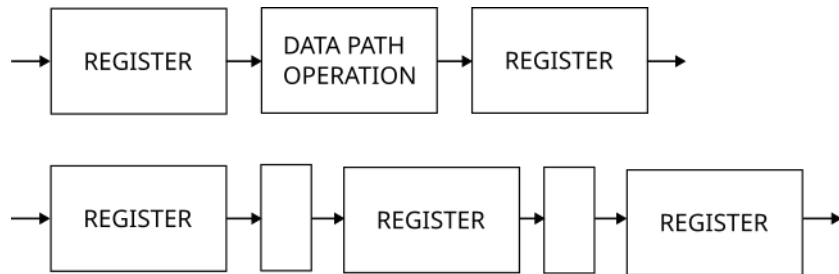The idea behind pipelining is to take a large data-path operation that is currently executed over one clock cycle and break it up into smaller operations that are executed over multiple shorter clock cycles.



The image above shows how the pipelining looks like. In the first line of the image there is logical block with with two registers. This block slows down the clock frequency for example to 500 MHz. We assume that the operations in the middle block can be splitted into two blocks. This operation should increase clock frequency for example to 1GHz.



Parallel computing

Assume that we want to implement $Y = A + B + C + D$ function in FPGA.

The adder can be presented as block with 4 inputs and 1 output.

Making adder with 4 input could be difficult

to realize in FPGA. We can decompose


function Y and present it as

$Y = ((A+B)+C)+D$ but it is still a sequential

calculations. There is other decomposition

$Y = (A+B) + (C+D)$. $(A+B)$ and $(C+D)$ can be

performed in parallel.

 




Pipelined adder

In this way we can achieve a pipelined adder circuit.

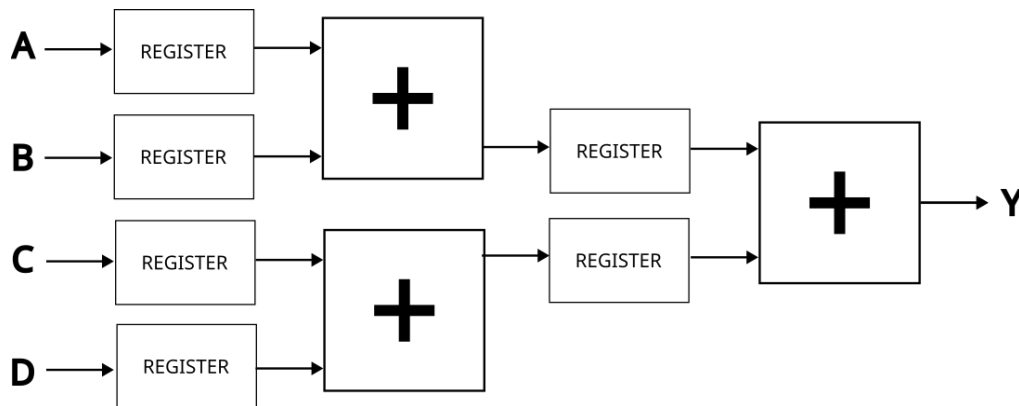The adder from the previous slide could add 4 signals in 1 clock's cycle. The adder presented below can do the same calculations in 2 cycles but it can do it with higher clock's frequency.





Application of RTL design

- GPU performs calculations on the data stream, pipelining is an excellent solution for these types of applications. The use of pipelining and RTL architecture increases GPU throughput by increasing the clock frequency
- NPU also performs computing on the data stream. Real-time applications like objects recognition or object tracking require high throughput and a fast clock.
- CPU is specific case. It uses some instructions that use pipelining but pipelining is used used by the processor in instruction handling




Pipelining in CPU

In non-pipelined version of CPU, as you can see, the CPU is waiting to end instruction before starting the next one.

Pipelined version doesn't wait to end of the last instruction.

 It starts handle the instruction after instruction in every cycle.






Pipelined adder

16 bit adder can be implemented with 4-bit adder based on slice.

This pipeline has 4 stages, so need

four cycles to give the result.

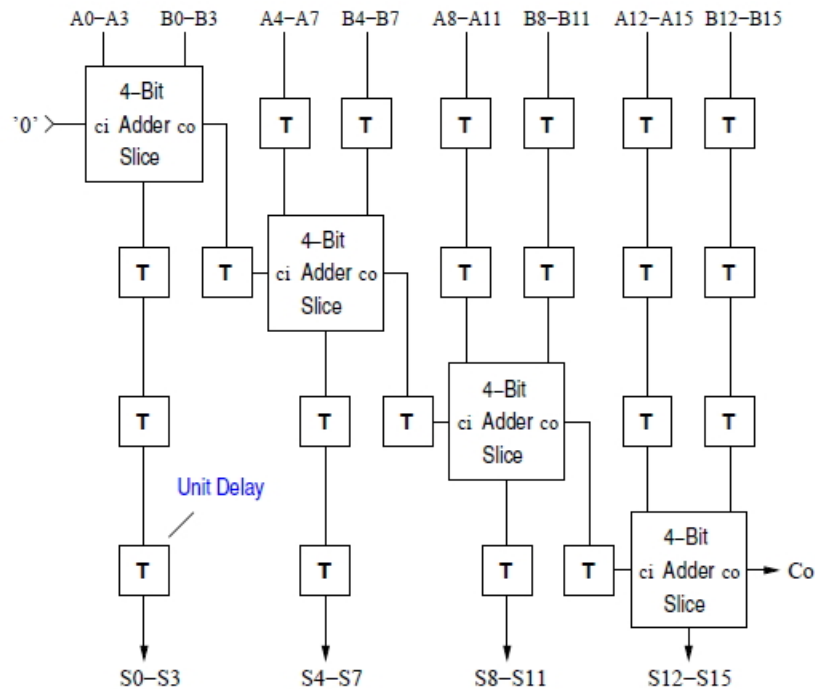



Advantages of RTL implementation

- Improves throughput
- Easy to verify
- Easy to debug
- Easy to understand
- Perfect for data streams



Disadvantages of RTL implementation

- Loss of initial clock cycles
- Requires algorithm/problem decomposition
- Pipelining is not suitable for single data
- More data paths in one block require synchronization



Synchronization

Look at the problem $Y=A*B+C$.

How to implement it using pipelining?

Because the operations are not independent, multiplication must be done first and then addition. We cannot directly send C signal to adder because we don't know the result of multiplication. So signal C must be synchronized with the result of multiplication. It can be done by adding additional register that will delay signal C in data path.



Increasing frequency

If there is more than one path in the design and one generates a pipeline and the other does not, we can optimize the circuit. Assuming that one of these paths determines the clock speed, you can divide the activities performed on this path into stages to create a pipeline. It should increase clock frequency.



Avoiding mistakes

- Try to implement and keep digital blocks as small as possible
- Avoid behavioral architecture
- Use behavioral description to describe small blocks like MUXes, logic gates, etc. It doesn't make sense to describe them as logical equations
- Before you use pipelining, think about whether it is profitable. Otherwise, you may waste unnecessary time.



Behavioral vs RTL synthesis

In some experiments behavioral design gives better synthesis results than RTL design.

| Description | Behavioral Design | RTL Design |
|-------------------------------|-------------------|---------------------|
| Behavioral | ~3200 vhdl lines | No behavioral model |
| RTL VHDL | 9311 vhdl lines | 10250 vhdl lines |
| Number of Gates | 28500 gates | 27000 gates |
| # of Partitioning modules | 7 modules | 15 modules |
| Design effort (Persons/Month) | 8 P/M | 25 P/M |

Source [Comparing RTL and behavioral design methodologies in the case of a 2M-transistor ATM shaper](#)



Project Simulation Phases

Depending upon the amount of design innovation in a new project, the emphasis on the different simulation phases may vary, but generally they consist of

- debugging.
- regression.
- recreating hardware problems.
- To this set of usual simulation phases, we add simulation performance profiling between the debugging and regression phases.



Debugging Phase

As engineers begin their first simulations of their designs, simulations invariably fail to pass their tests due to design bugs. The number of bugs is generally proportional to the size of the simulated design and the amount of innovation applied in the new design.



Regression Phase

The regression simulation phase begins when a design passes nearly all of its tests.

During this phase, the project uses as much computing horsepower as it can find to run as many different directed, directed random, and random simulations as it can on all the possible configurations of the simulated model.



Recreating Hardware Problems

An important application of RTL simulation is recreating design problems that show up in the hardware lab testing. The first step is crafting the test that duplicates the hardware problem in simulation. The next step is devising the logic change that fixes the problem, then running the test to show that the problem is fixed for that test. The test can then join the regression suite of tests.



Debugging and regression model differences

| | Debugging Phase | Regression Phase |
|--|--|---|
| Verilog compilation | Standard vendor model | Cycle-based optimizations |
| Internal signal accessibility. | Full accessibility to all registers and intermediate combinational values. | Access to interface buses and selected registers. |
| Waveform viewing trace file output | Optimized for size and specific waveform viewer. | None. |
| Diagnostic logging information output | Full diagnostic logging information available | Error detection only |
| PLI C/C++ code | Debug mode enabled in compile, minimal optimization level. | No debug in compile, maximum optimization levels |